

Relay Shield v3.0 SKU:103030009



The Relay Shield provides a solution for controlling high current devices that cannot be controlled by Arduino's Digital I/O pins due to current and voltage limits.

The Relay Shield features four high quality relays and provides NO/NC interfaces, four dynamic LED indicators to show the on/off state of each relay, and the standardized shield form factor to provide a smooth connection to the Arduino/Seeeduino board or other Arduino compatible boards.

Features

- Arudino Uno/Leonardo/Seeeduino compatible; Other board or microcontroller via jumper cables
- Interface via digital I/O pins 4,5,6, and 7
- Relay screw terminals
- Standardized shield shape and design
- LED working status indicators for each relay
- High quality relays
- COM, NO (Normally Open), and NC (Normally Closed) relay pins for each relay
- Update pin SCL, SDA, IOREF, NC.

Specification

Item	Min	Typical	Max	Unit
Supply Voltage	4.75	5	5.25	VDC
Working Current	8	-	250	mA

Item	Min	Typical	Max	Unit
Switching Voltage	-	-	30	VDC
Switching Current	-	-	8	A
Frequency	-	1	-	Hz
Switching Power	-	-	70	W
Relay Life	100,000	-	-	Cycle
ESD contact discharge	-	±4	-	KV
ESD air discharge	-	±8	-	KV
Dimension	-	68.7X53.5X30.8	-	mm
Net Weight	-	55±2	-	g
Package size	-	100X67X32	-	mm
Gross Weight	-	77	-	g

!!!Cautions 1. Please place 2 layers of electrical tape on the top of the Arduino's usb connector. This will prevent the relay shield from making contact. 2. Do not operate voltage more than 35V DC.

Compatibility


We have produced a lot of extension board that can make your platform board more powerful, however not every extension board is compatible with all the platform board, here we use a table to illustrate how are those boards compatible with platform board.

!!!note Please note that "Not recommended" means that it might have chance to work with the platform board however requires extra work such as jump wires or rewriting the code. If you are interested in digging more, welcome to contact with techsupport@seeed.cc.

Click to see full picture

	Arduino Uno Seeeduino v4.2	Arduino Mega Seeeduino Mega	Zero(m0) LoraWan	Arduino Leonardo Seeeduino Lite	Arduino 101	Arduino Due 3.3v	Intel Edison 5v	Linkit One
2.8'' TFT Touch Shield V2.0	bmp non support	bmp non support	Not recommended	bmp non support	Not recommended	Not recommended	Not recommended	Not recommended
Base Shield V2	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes
Camera Shield	Only Pin234567	Hardware Serial OK	Not recommended	Not recommended	Yes	Hardware Serial OK	No	No
EL Shield	Yes	Yes	No	Yes	No	No	No	No
Energy Shield	Yes	Yes	Yes	Yes	Yes	Yes	Yes	No
GPRS Shield	Not recommended	Not recommended	Yes	Yes	Yes	Not recommended	Yes	No need
Motor Shield V2.0	Yes	Stepper motor only	No	Yes	Stepper motor only	Stepper motor only	No	No
Music Shield V2.0	Yes	Yes	Not recommended	Yes	Yes	Yes	Yes	Yes
NFC Shield V2.0	Yes	Yes	Yes	Yes	Yes	Yes	No	Yes
Protoshield Kit for Arduino	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes
RS232 Shield	Yes	Yes	No	Yes	No	No	No	No
Relay Shield V3.0	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes
SD Card Shield V4.0	Yes	Yes	Not recommended	Yes	Yes	Yes	No	No
Seeed BLE Shield V1	Yes	Not recommended	Not recommended	Yes	No need	Not recommended	Not recommended	No need
W5500 Ethernet Shield	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes
Wifi Shield(Fi250) V1.1	Not recommended	Not recommended	Not recommended	Yes	Yes	Not recommended	No need	No need
Wifi Shield V2	Yes	Not recommended	Not recommended	Yes	Yes	Not recommended	No need	No need
XBee Shield V2	Yes	Not recommended	Not recommended	Yes	Yes	Not recommended	Not recommended	Not recommended

Shield Interface Description

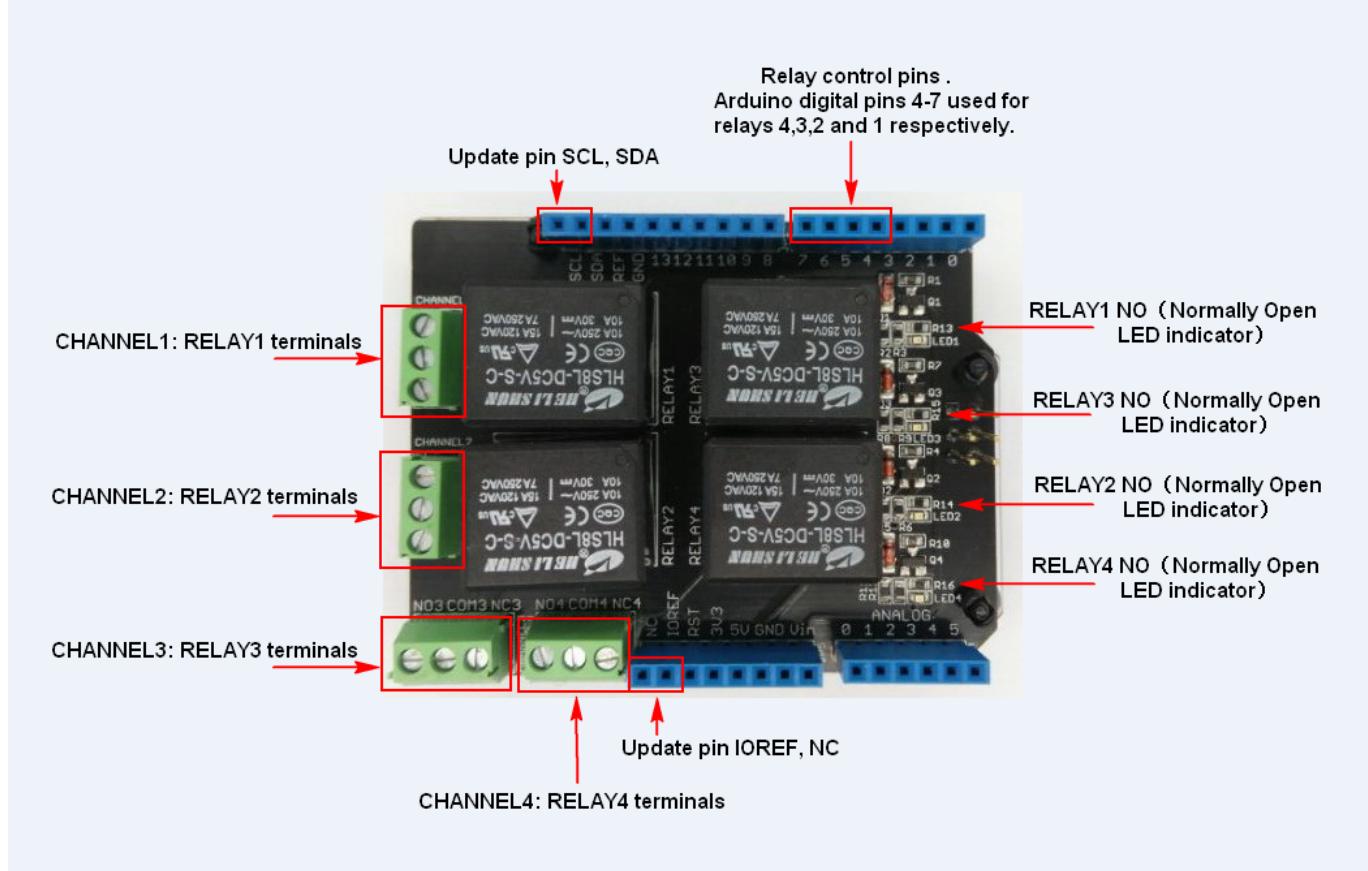

- Digital 4 – controls RELAY4's COM4 pin (located in J4)
- Digital 5 – controls RELAY3's COM3 pin (located in J3)
- Digital 6 – controls RELAY2's COM2 pin (located in J2)
- Digital 7 – controls RELAY1's COM1 pin (located in J1)

J1 Interface/Terminal Pin Description:

- **COM1 (Common Pin)** : The relay pin controlled from the digital pin.
- **NC1 (Normally Closed)**: This terminal will be connected to COM1 when the RELAY1 control pin (Digital 7 I/O pin) is set low and disconnected when the RELAY1 control pin is set high.
- **NO1 (Normally Open)**: This terminal will be connected to COM1 when the RELAY1 control pin (Digital 7 I/O pin) is set high and disconnected when the RELAY1 control pin is set low.

**Terminals J2-4 are similar to J1 except that they control RELAY2-RELAY4 respectively. **


!!!Note Only four Arduino Digital I/O pins, pins 4-7, are required to control the four different relays. Additionally the 5V and two GND Arduino pins are also required to power up the Relay Shield.

Relays Operation/Tutorial

Relays are basically electromagnetic switches: when the relay is energized by the control circuit (i.e. when a voltage and current is applied to the coil), the current and coil create a magnetic field which is able to attract the COM terminal towards the NO terminal, when the control circuit removes the applied voltage and current the COM terminal returns to contact the NC terminal due to a mechanical force (usually a spring).

Some practical relay applications include: control of high voltage using low voltage, motor control, remote control, anti-heating alarm, automatic temperature alarm, incubators and so on.

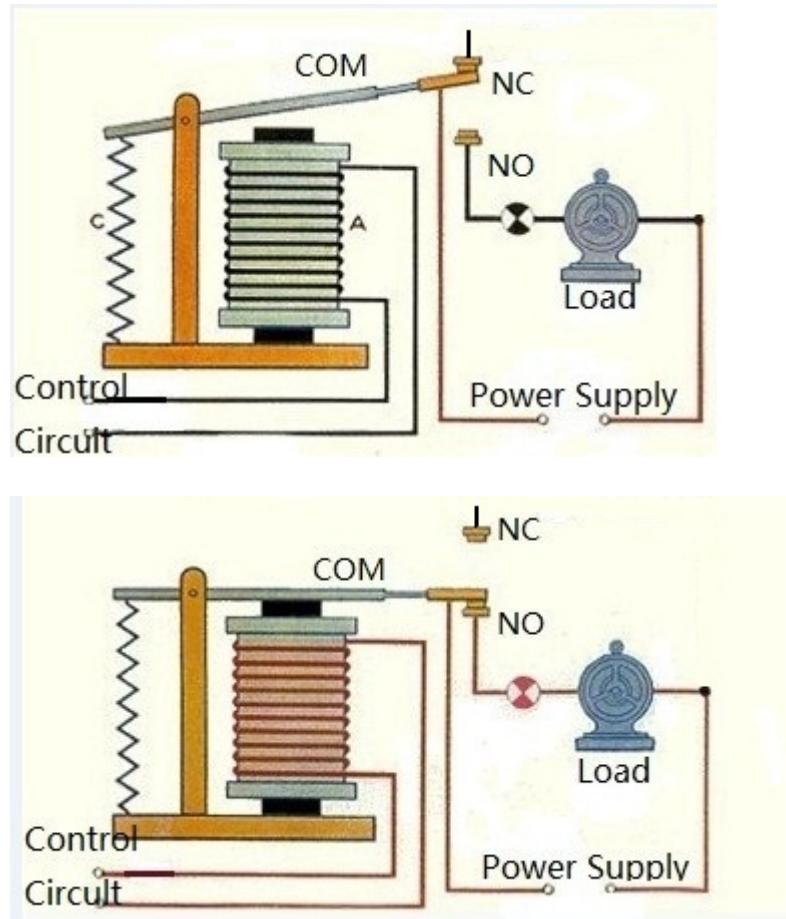A motor control application with one relay and one motor is shown below:





In the case of the Relay Shield, the two "Control Circuit" terminals for each of the four relays are controlled by only one Arduino Digital I/O pin. Pins 4, 5, 6, and 7 control relays 4, 3, 2, and 1 respectively.

Relay Shield Example(s)/Usage

Now that you know how a relay works internally, let us show you how to use the Relay Shield.

Example #1: DC Motor Control

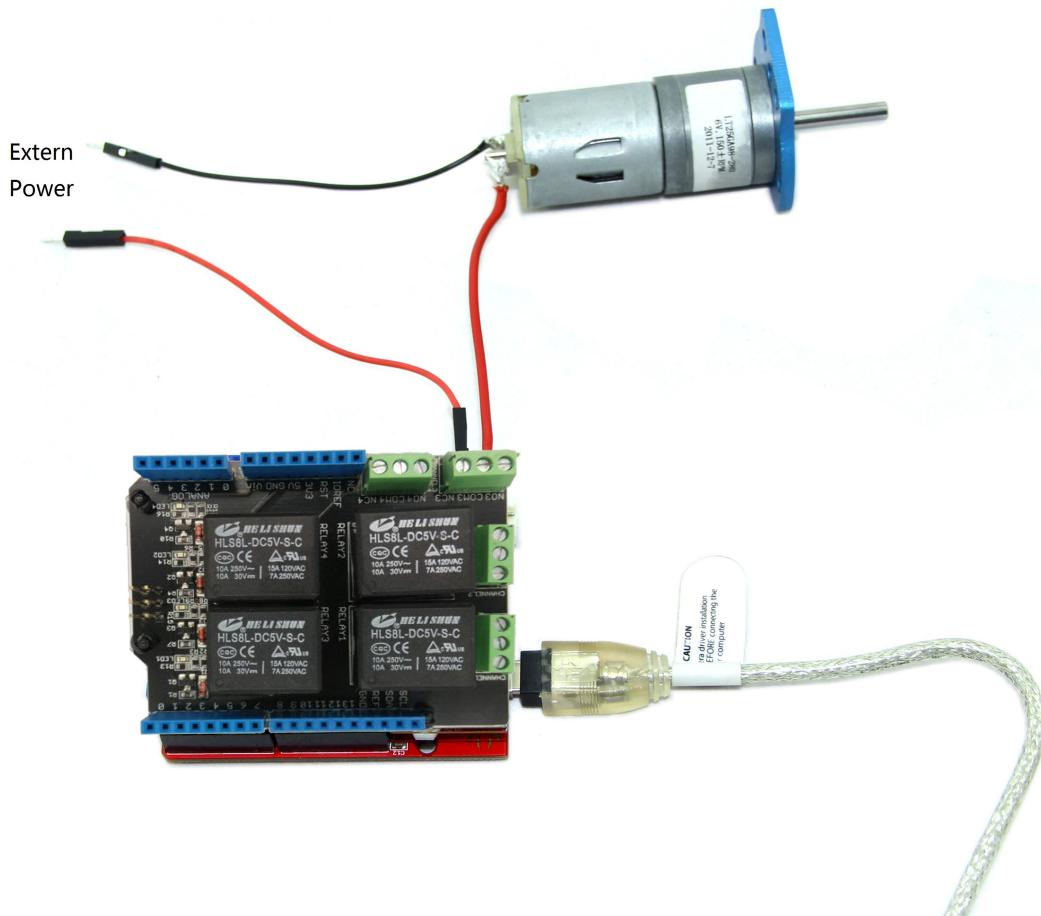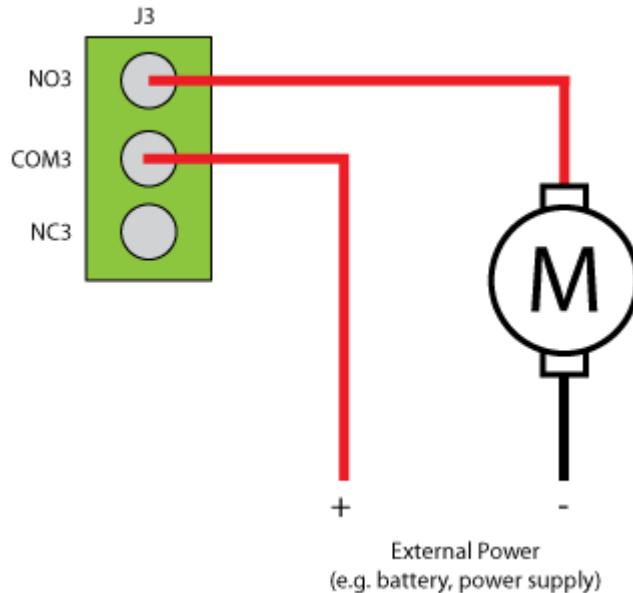- 1.Stack the Relay Shield onto the Arduino development board.
- 2.Connect Arduino to your PC using a USB cable.
- 3.We will use RELAY3 to control the DC motor. Connect the DC motor and Relay Shield as shown in the schematic and figure below:



!!!Note The external power supply in the figure above can be a battery or power supply. The external supply must be able to provide enough current and be set to the correct voltage for the motor. In our testing, we used a lithium battery as the external power supply for the motor.

4.Start the Arduino IDE and upload the following code to the Arduino board:

```
int MotorControl = 5;      // Digital Arduino Pin used to control the motor

// the setup routine runs once when you press reset:
void setup() {
```

```

// declare pin 5 to be an output:
pinMode(MotorControl, OUTPUT);
}

// the loop routine runs over and over again forever:
void loop() {
    digitalWrite(MotorControl,HIGH); // NO3 and COM3 Connected (the motor is running)
    delay(1000); // wait 1000 milliseconds (1 second)
    digitalWrite(MotorControl,LOW); // NO3 and COM3 Disconnected (the motor is not
running)
    delay(1000); // wait 1000 milliseconds (1 second)
}


```

When you have uploaded the code to your Arduino/Seeeduino board the motor should run one second, stop for another second and repeat the process indefinitely. When the motor is running (NO3 and COM3 are connected), the NO3 LED indicator will be lit.

Example #2: How to Use More Than One Relay Shield With Only One Arduino/Seeeduino Board

Because the Relay Shield uses digital pins on the Arduino to control each the relays, more than one Relay Shield can be used with the same Arduino board, to do so simply follow these steps:

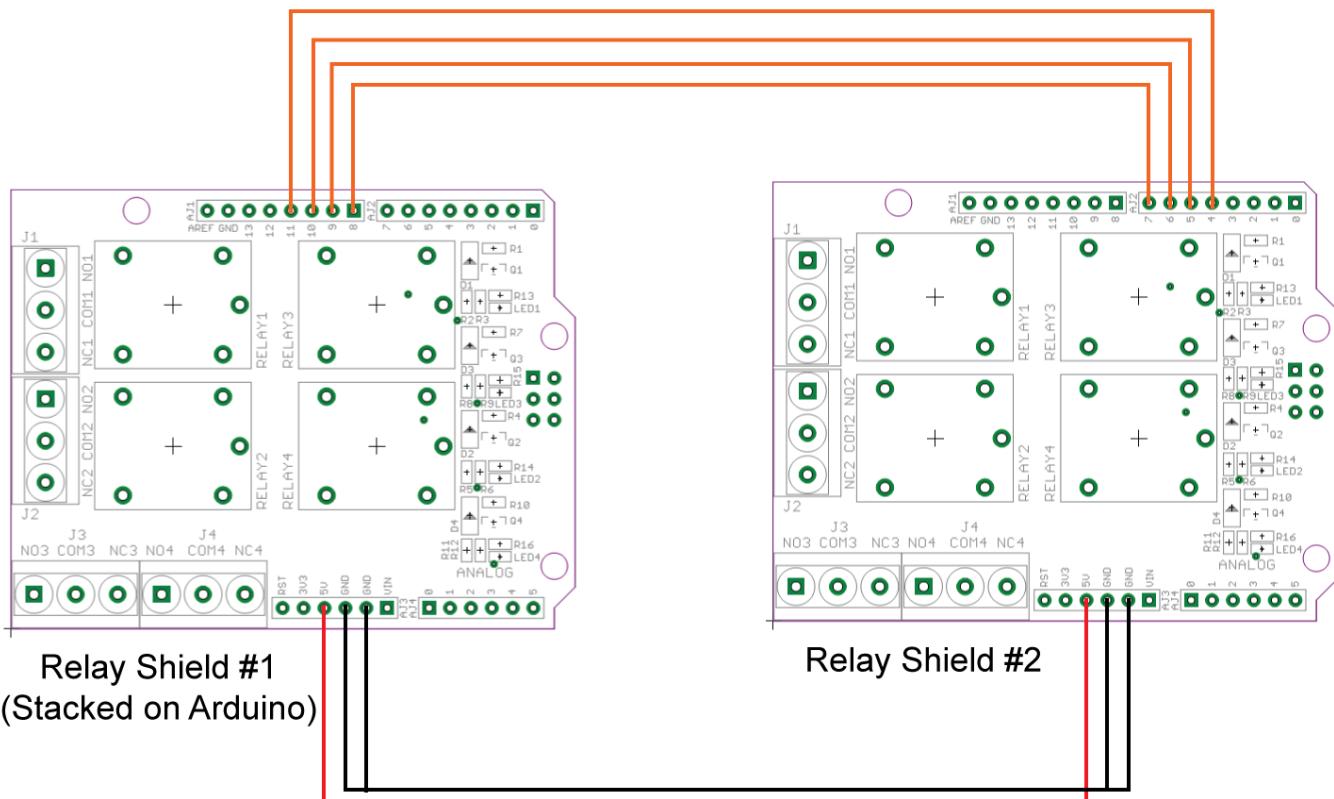- 1.Stack one of the Relay Shields (let's call this one Relay Shield #1) onto the Arduino development board
- 2.Connect another Relay Shield (let's call this one Relay Shield #2) using jumper cables/wires to Relay Shield #1 as shown in the figure below:



- Relay Shield #1 GND pin is connected to Relay Shield #2 GND pin
- Relay Shield #1 5V pin is connected to Relay Shield #2 5V pin

- Relay Shield #1 Digital Pins 8, 9, 10, and 11, are connected to Relay Shield #2 Digital Pins 7, 6, 5, and 4 respectively.

3. Now you can control relays 1, 2, 3, and 4 in Relay Shield #2 using the Arduino's 8, 9, 10, and 11 digital I/O pins. See sample code below for controlling RELAY1 in Relay Shield #2:

```
int relay1inShield2 = 8;      // Digital Arduino Pin 8 is used to control relay 1 in
Relay Shield #2

// the setup routine runs once when you press reset:
void setup() {
    // declare pin 8 to be an output:
    pinMode(relay1inShield2, OUTPUT);
}

// the loop routine runs over and over again forever:
void loop() {
    digitalWrite(relay1inShield2,HIGH); // relay is energized (NO is connected to
COM)
    delay(1000); // wait 1000 milliseconds (1 second)
    digitalWrite(relay1inShield2,LOW); // NO is disconnected from COM
    delay(1000); // wait 1000 milliseconds (1 second)
}
```

Related Reading

- [FAQ of Relay Shield](#)

Resource

- [Relay Shield v3.0](#)

Tech Support

Please submit any technical issue into our [forum](#) or drop mail to techsupport@seeed.cc.